



**COLORADO SCHOOL OF MINES  
ELECTRICAL ENGINEERING DEPARTMENT**

**EENG 577**

**ADVANCED ELECTRICAL MACHINE DYNAMICS FOR  
SMART-GRID SYSTEMS**

**M1-P2 Single & Three-Phase Power**

## Objectives

### I. Single Phase Power

- **Power concepts:**

- ✓ instantaneous power,
- ✓ average power, (real power);  $P$  (W)
- ✓ reactive power, (imaginary power);  $Q$  (VAR)
- ✓ complex power,  $S = P + jQ = |S| \angle \theta$  (VA)
- ✓ apparent power =  $|S|$  (VA)
- ✓ power factor angle =  $\theta$
- ✓ Power factor =  $\cos(\theta)$

- **Power Triangle:**

- ✓ Relationships among power concepts.


### II. Three-Phase Power

# Given

In a **constant frequency ac** system

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

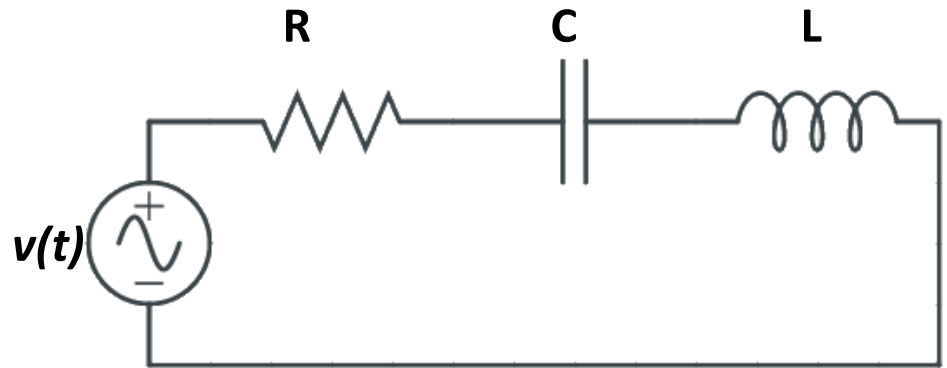

Root Mean Square (RMS) voltage of sinusoid (V):

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} = \frac{V_m}{\sqrt{2}}$$

As such,  $v(t)$  is expressed in terms of the Root RMS value as follows:

$$v(t) = \sqrt{2} V_{rms} \cos(\omega t + \theta_v)$$

# Instantaneous power:

## Given

$$p(t) = v(t) i(t)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$\text{Note: } \cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

$$p(t) = v(t)i(t)$$

$$= [V_m \cos(\omega t + \theta_v)] [I_m \cos(\omega t + \theta_i)]$$

... (lots of trigonometry) ...

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t \\ - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$


## Rewrite

$$p(t) = P + P \cos 2\omega t - Q \sin 2\omega t$$

where

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$
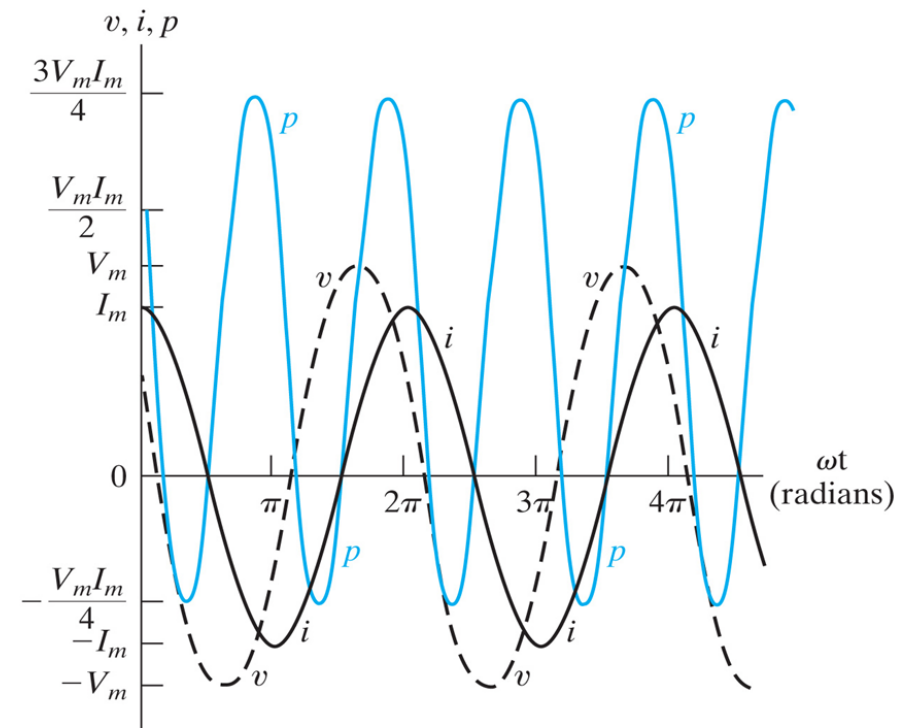
$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$



Copyright © 2008 Pearson Prentice Hall, Inc.



ELECTRICAL ENGINEERING DEPARTMENT  
COLORADO SCHOOL OF MINES

## Instantaneous power, rewritten:

$$p(t) = P + P \cos 2 \omega t - Q \sin 2 \omega t$$

where  $P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$

and  $Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$

## Definitions:

**Power Factor Angle** =  $\theta = \theta_V - \theta_I$

**Power Factor**, PF =  $\cos\theta$

**P** is the average (or real) power and has the unit Watt [W]

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$$

**Q** is the reactive power and has the unit Volt-Ampere-Reactive [VAR]

## Complex Power (Definition)

$$\bar{S} = P + jQ = S \angle \theta$$

- For a **resistor** in the presence of an AC source, **voltage and current are in-phase!**

$$\cos(\theta_v - \theta_i) = \cos(0^\circ) = 1; \quad \sin(\theta_v - \theta_i) = 0$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m I_m}{2}; \quad Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = 0$$

Note

$$p(t) = v(t) i(t)$$

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

- For an **inductor** the **current lags the voltage by 90°**:

$$\cos(\theta_v - \theta_i) = \cos(90^\circ) = 0; \quad \sin(\theta_v - \theta_i) = \sin(90^\circ) = 1$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = 0; \quad Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = \frac{V_m I_m}{2}$$

- For a **capacitor**, the **current leads voltage by 90°**:

$$\cos(\theta_v - \theta_i) = \cos(-90^\circ) = 0; \quad \sin(\theta_v - \theta_i) = \sin(-90^\circ) = -1$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = 0; \quad Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) = -\frac{V_m I_m}{2}$$

# Complex Power

$$\bar{S} = P + jQ = S \angle \theta$$

$$\bar{S} = \bar{V} \bar{I}^*$$


*Note the apparent power  $S$  is the magnitude of the complex power where  $S=VI$  in VA*

*As such*

$$P = S \cos \theta$$

$$Q = S \sin \theta = S \sqrt{1 - pf^2}$$

Some utilities charge for the Apparent Power:  
 **$|S|=VI$**  in VA

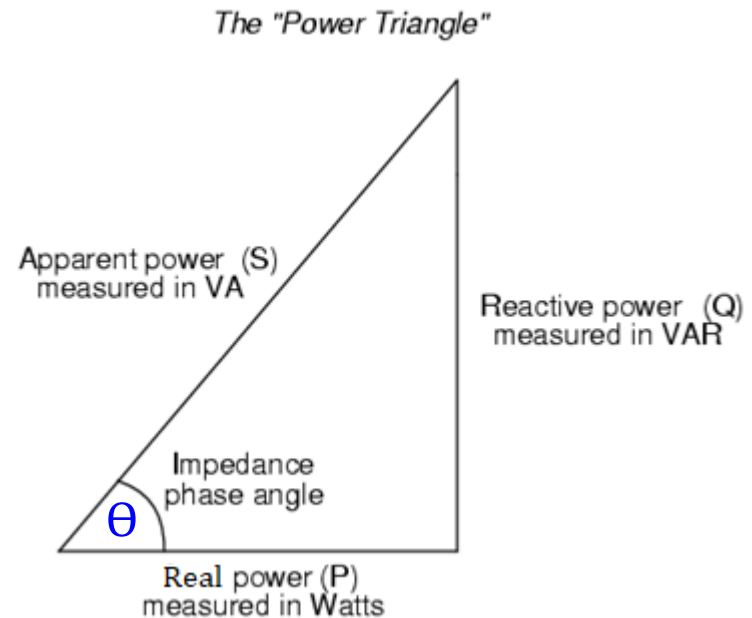

# Power Consumption in Devices

Resistors only consume real power

$$P_{\text{Resistor}} = |I_{\text{Resistor}}|^2 R$$

$P_{\text{Resistor}} > 0$  Consume

Inductors only consume reactive power

$$Q_{\text{Inductor}} = |I_{\text{Inductor}}|^2 X_L \quad ; X_L = \omega L$$

$Q_{\text{Inductor}} > 0$  Consume

Capacitors only generate reactive power

$$Q_{\text{Capacitor}} = -|I_{\text{Capacitor}}|^2 X_C \quad X_C = \frac{1}{\omega C}$$

$$Q_{\text{Capacitor}} = -\frac{|V_{\text{Capacitor}}|^2}{X_C}$$


$Q_{\text{Capacitor}} < 0$  Generate



## **THREE-PHASE CIRCUITS**

- **Three Phase Circuits**
- **Three Phase Connections**
- **Source/Load   Delta-Y connections**
- **Power Relationships**

# THREE PHASE CIRCUITS

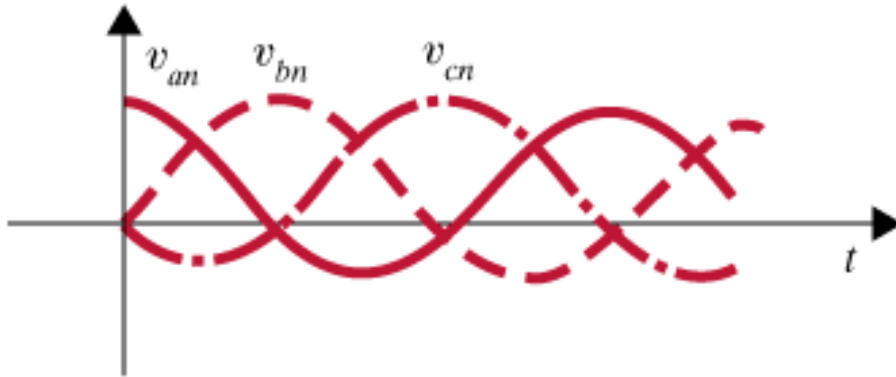


Instantaneous Phase Voltages


$$v_{an}(t) = V_m \cos(\omega t)(V)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)(V)$$
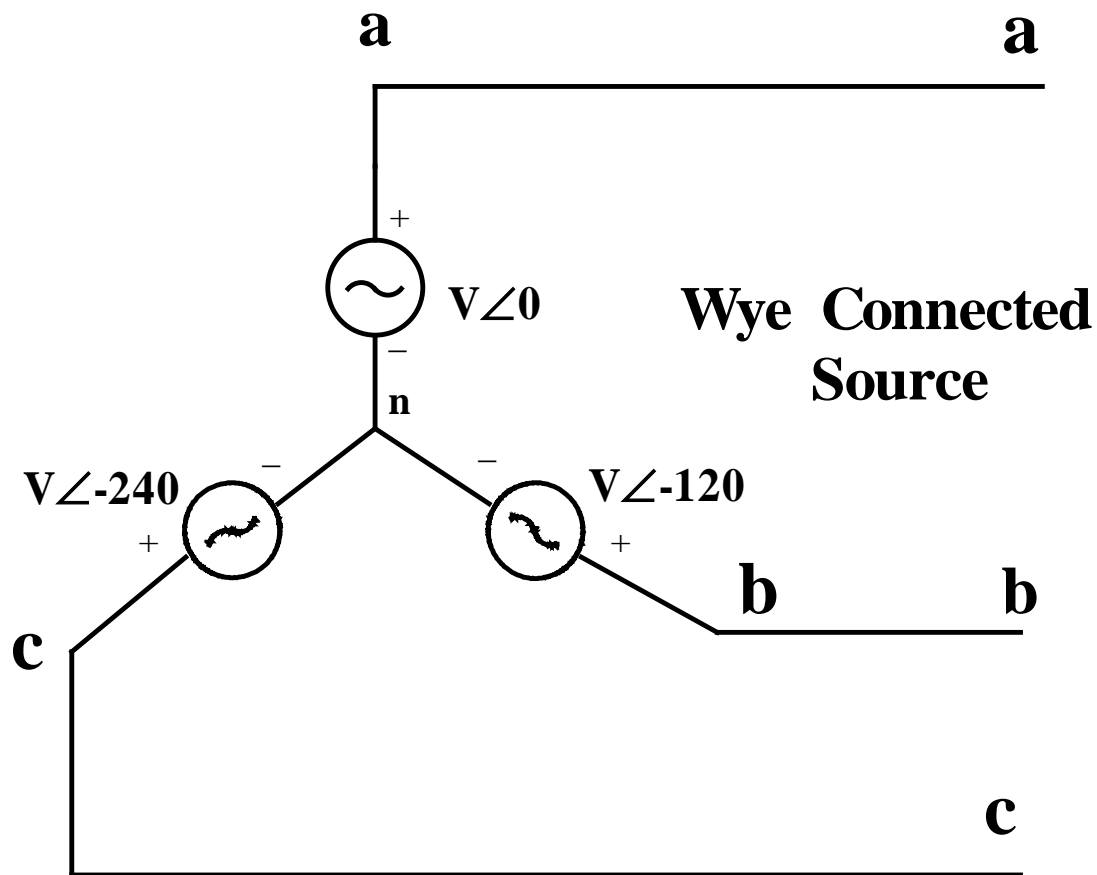
$$v_c(t) = V_m \cos(\omega t - 240^\circ)(V)$$



# Delta Source

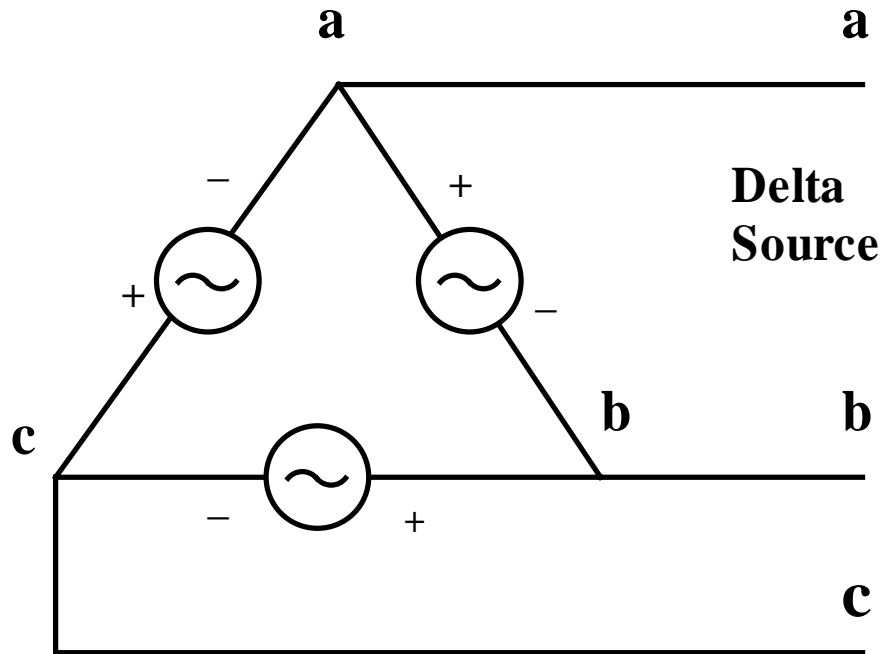


$$\mathbf{V}_{ab} = |V_{ab}| \angle 0$$


$$V_{bc} = V_{ab} \angle -120$$

$$V_{ca} = V_{ab} \angle -240$$


# Wye – Wye System

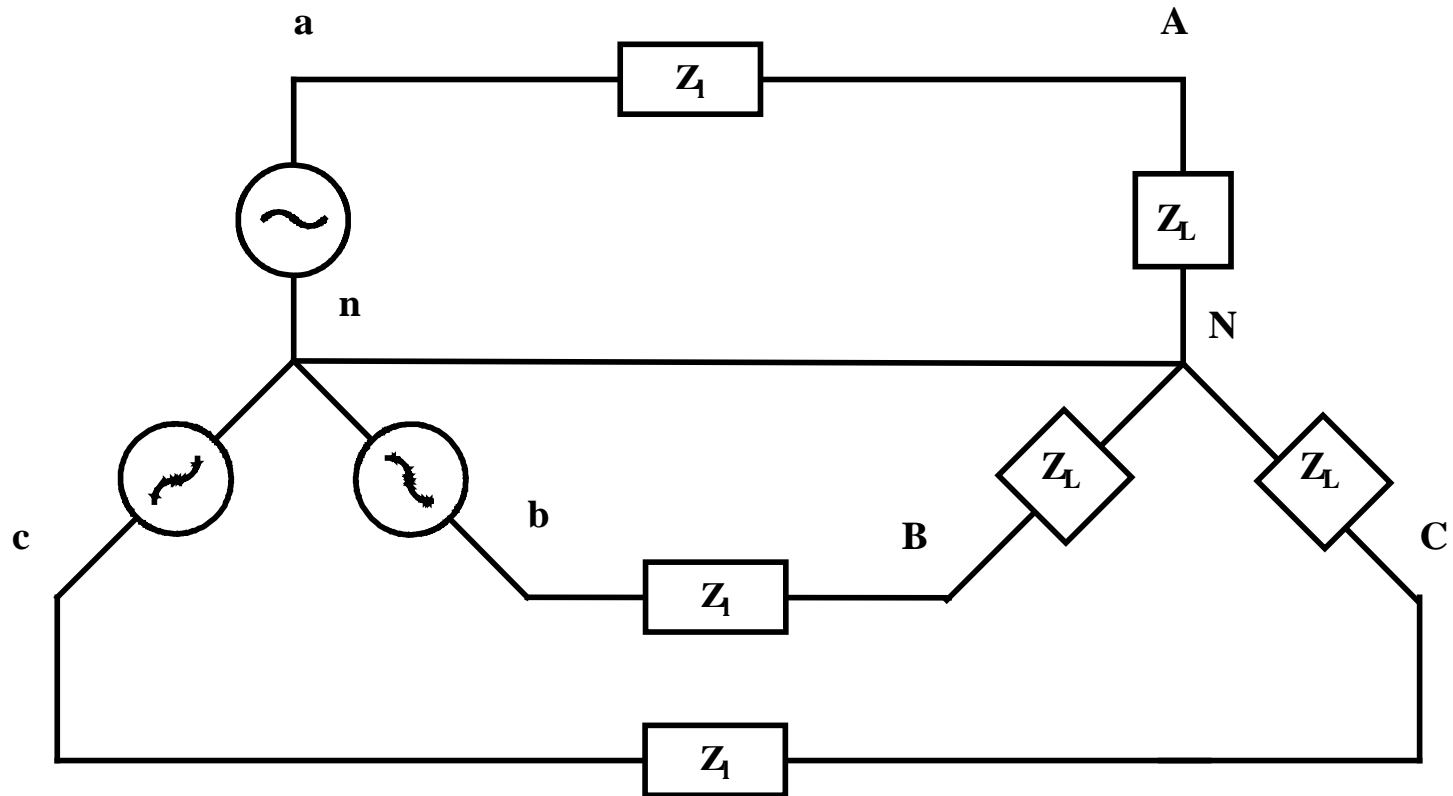


# Delta – Delta System

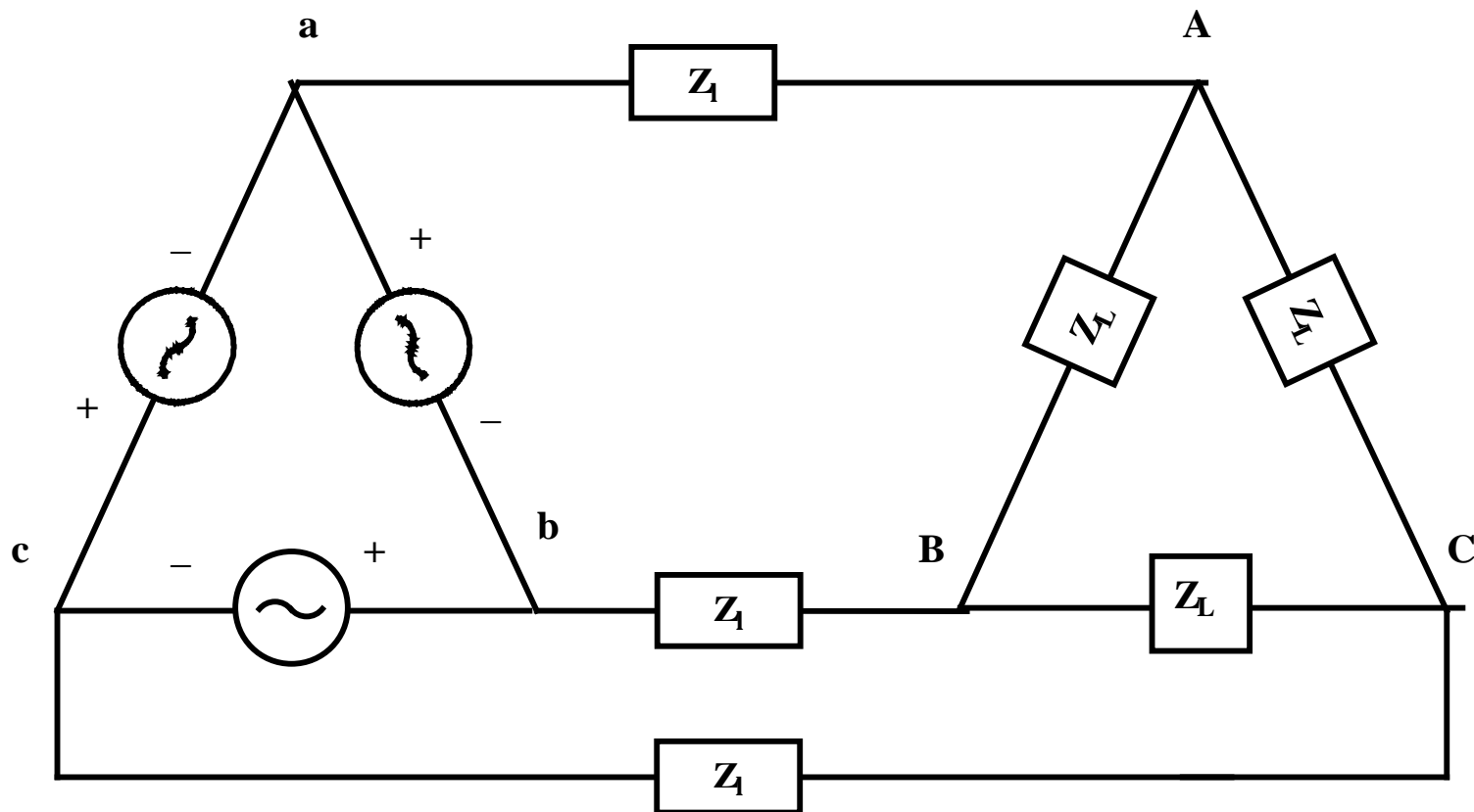


# Delta – Wye System

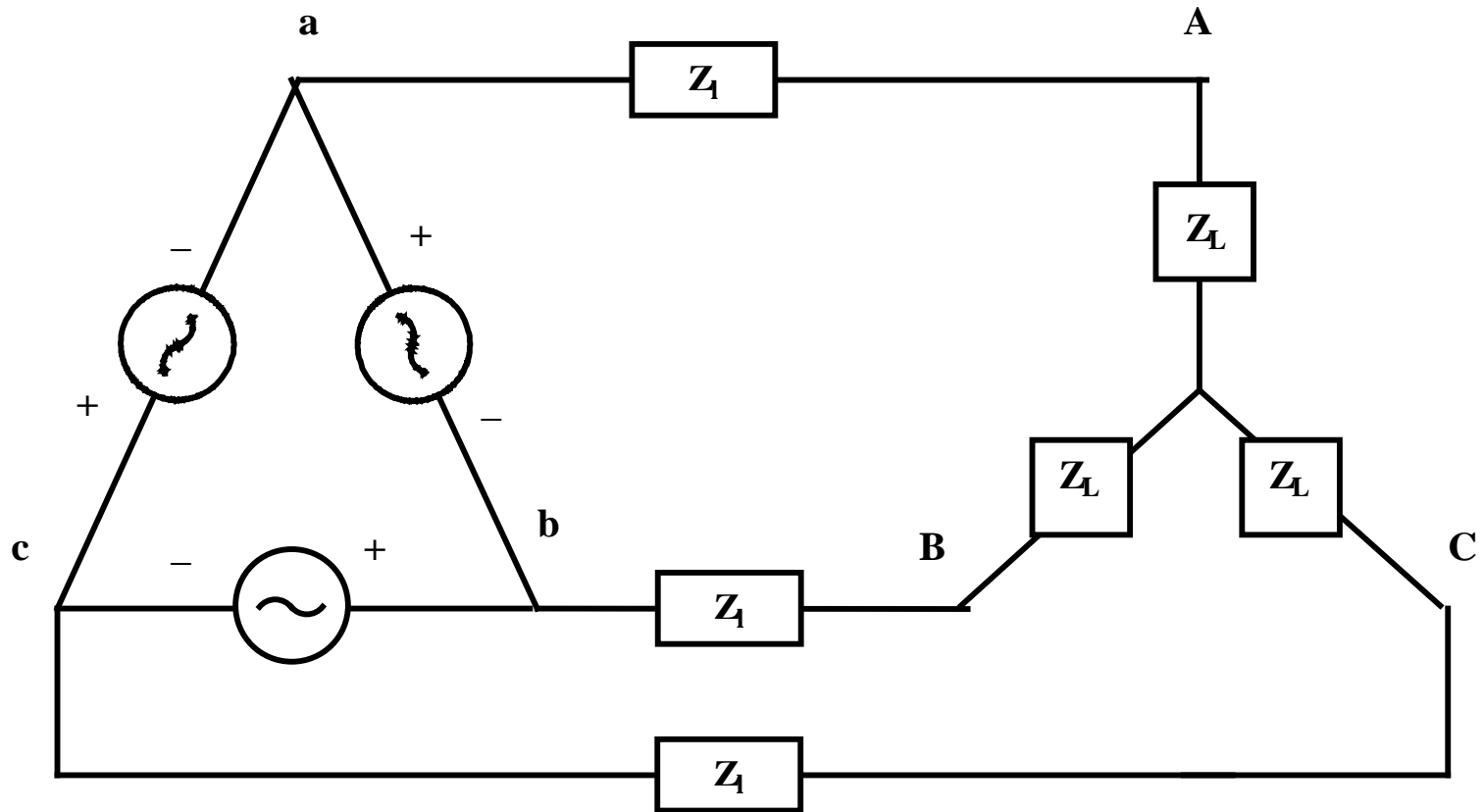

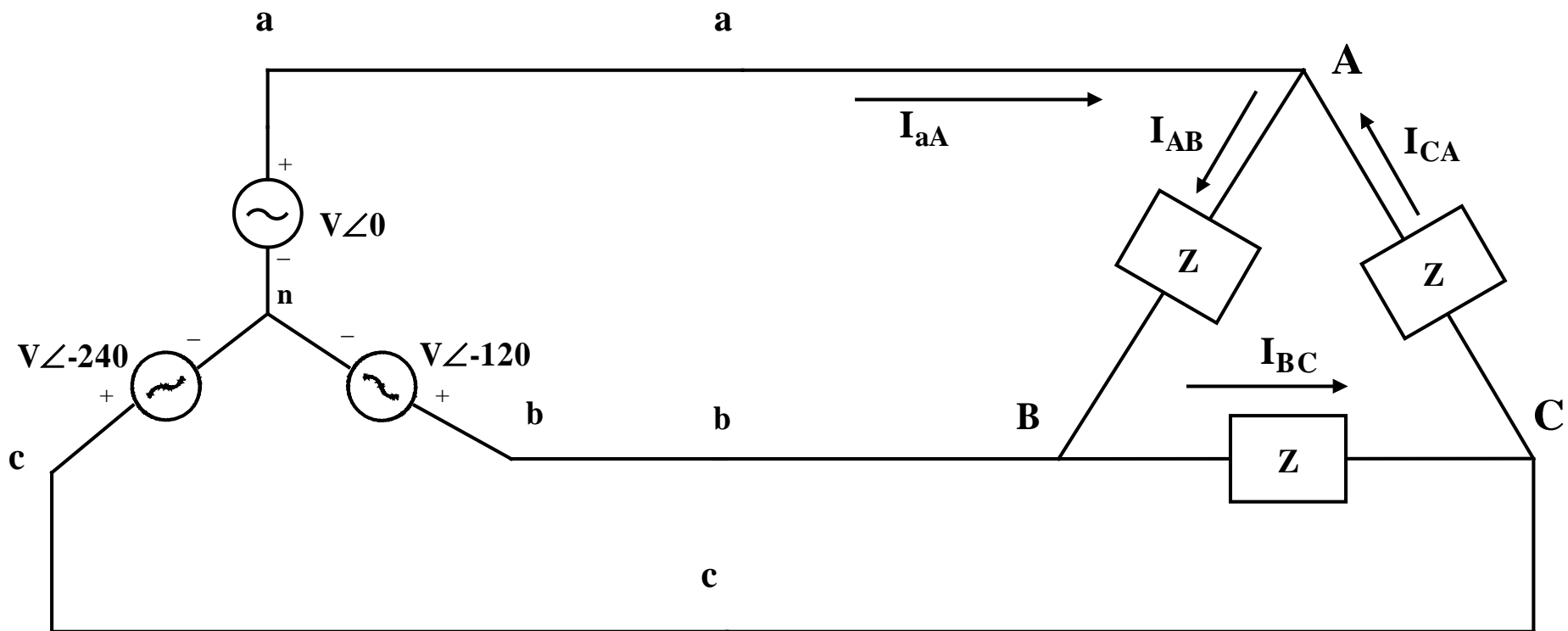




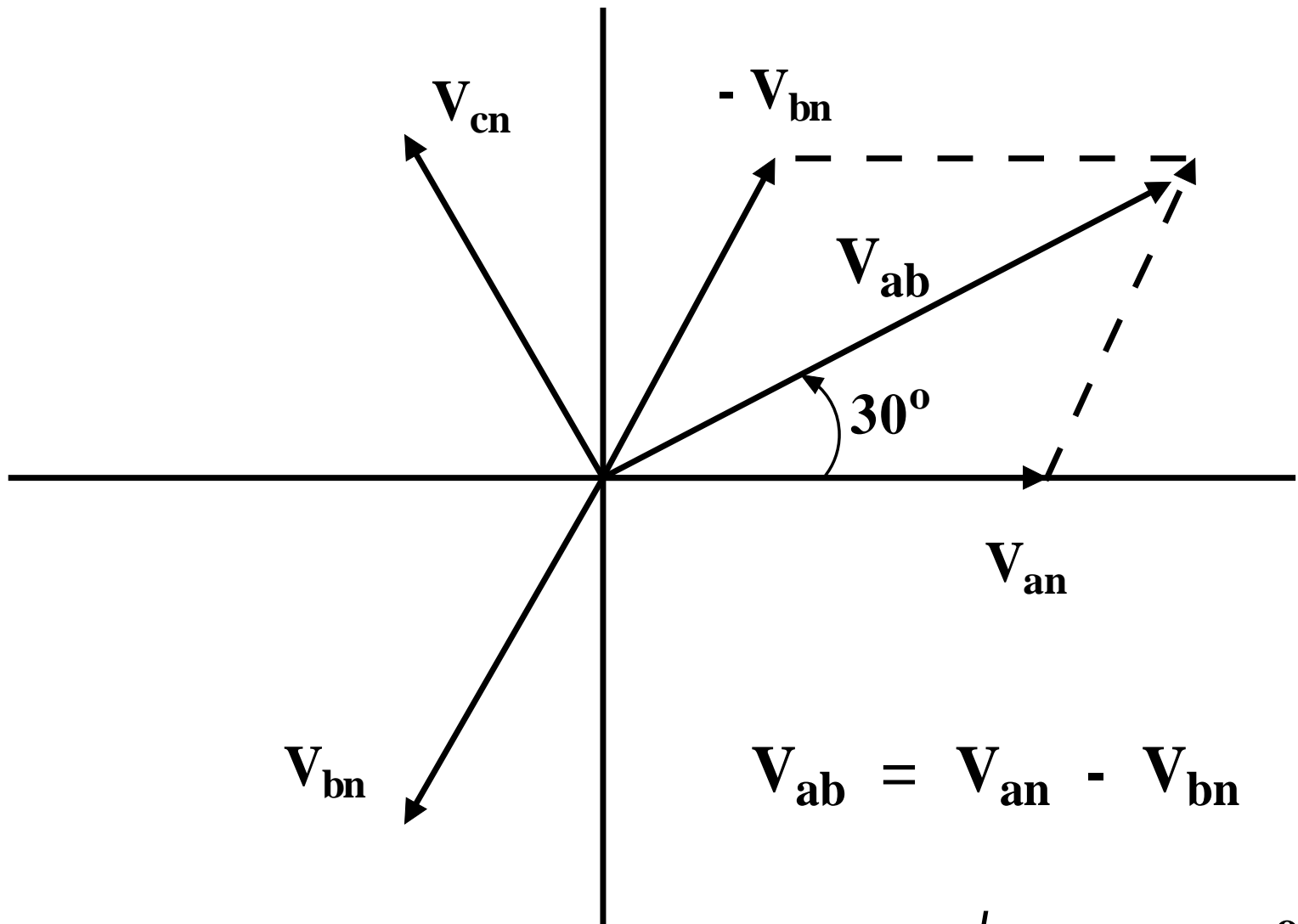

$$V_{ab} = V_{an} - V_{bn}$$
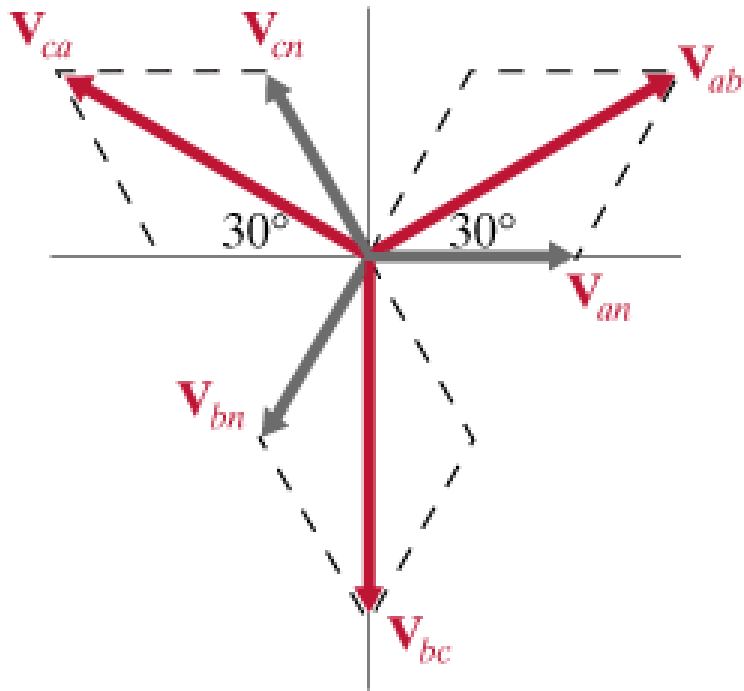
$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ$$



(b)

$$\begin{aligned}
 V_{ab} &= V_{an} - V_{bn} \\
 &= |V_p| \angle 0^\circ - |V_p| \angle -120^\circ \\
 &= |V_p| (1 - (\cos 120 - j \sin 120)) \\
 &= |V_p| \left( \frac{1}{2} - j \frac{\sqrt{3}}{2} \right) \\
 &= \sqrt{3} |V_p| \angle 30^\circ
 \end{aligned}$$

$$V_{bc} = \sqrt{3} |V_p| \angle -90^\circ$$

$$V_{ca} = \sqrt{3} |V_p| \angle -210^\circ$$

$$V_L = \sqrt{3} |V_p| = \text{Line Voltage}$$

# INSTANTANEOUS POWER

Balanced 3–Phase Voltages

$$v_{an}(t) = V_m \cos(\omega t)(V)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)(V)$$

$$v_{cn}(t) = V_m \cos(\omega t - 240^\circ)(V)$$

Balanced 3–Phase Currents

$$i_a(t) = I_m \cos(\omega t - \theta)$$

$$i_b(t) = I_m \cos(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_m \cos(\omega t - \theta - 240^\circ)$$

Instantaneous power

$$p(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$


**Three-Phase Balanced Instantaneous Power**

$$p(t) = 3 \frac{V_m I_m}{2} \cos \theta (W)$$

$$p(t) = \frac{\sqrt{3}}{2} V_L I_L \cos \theta (W)$$

$\Delta \leftrightarrow Y$

Transformations

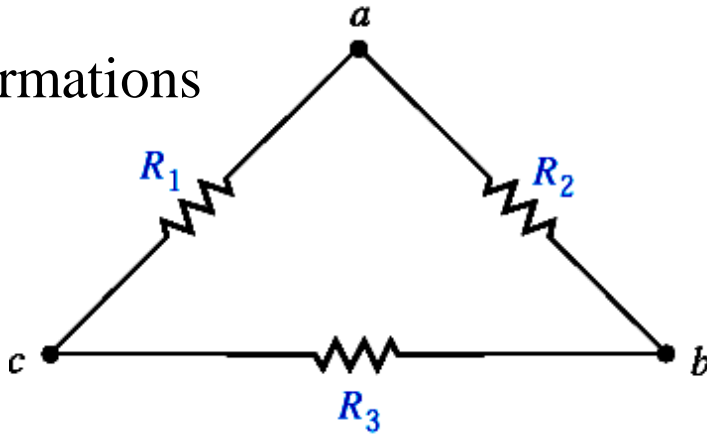


$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$\Delta \rightarrow Y$

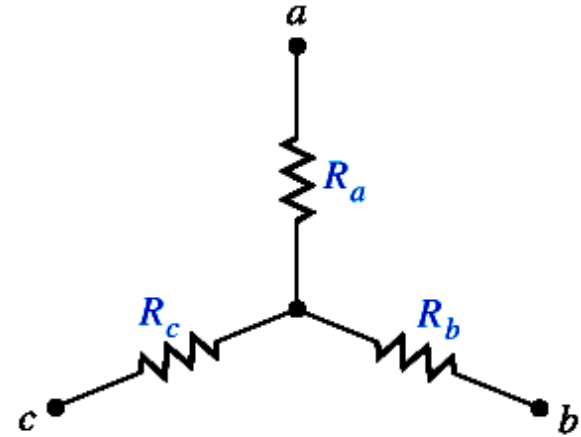

$$R_1 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$Y \rightarrow \Delta$

**Note:** In the **3-Phase Balanced case**, the above expressions are simplified as

$$R_1 = R_2 = R_3 \quad \& \quad R_a = R_b = R_c$$