



**COLORADO SCHOOL OF MINES
ELECTRICAL ENGINEERING DEPARTMENT**

EENG577 Advanced Electric Machine Dynamics for Smart-Grid Systems

M3 Project: Synchronous Generator-abc

Introduction

A 659 MVA, 4-Pole, 20 kV, 0.9 P.F., Double-Y Connected (with grounded neutral), 60 Hz turbogenerator, whose armature and field winding parameters (neglecting saturation) are summarized as follows:

r_s	=	$7.4 \times 10^{-4} \Omega$	r_f	=	0.0860Ω
r_{kd1}	=	$1.58 \times 10^{-4} \Omega$	L_{sv}	=	$0.05 \times 10^{-3} \text{ H}$
r_{kq1}	=	$1.227 \times 10^{-4} \Omega$	L_{mv}	=	$0.05 \times 10^{-3} \text{ H}$
L_{sa}	=	$1.95 \times 10^{-3} \text{ H}$	L_{ff}	=	$444 \times 10^{-3} \text{ H}$
L_{ma}	=	$0.80 \times 10^{-3} \text{ H}$	L_{akdm1}	=	$0.447 \times 10^{-3} \text{ H}$
L_{afm}	=	$26.1 \times 10^{-3} \text{ H}$	L_{akqm1}	=	$0.670 \times 10^{-3} \text{ H}$
L_{fkd1}	=	$5.05 \times 10^{-3} \text{ H}$	L_{kd1kd1}	=	$0.1254 \times 10^{-3} \text{ H}$
L_{kd1f}	=	$6.29 \times 10^{-3} \text{ H}$	L_{kq1kq1}	=	$0.3762 \times 10^{-3} \text{ H}$

PART I

1. Show a cross-section of the synchronous machine and draw corresponding winding schematic diagram and label all axes (a, b, c, f, d, and q) properly.

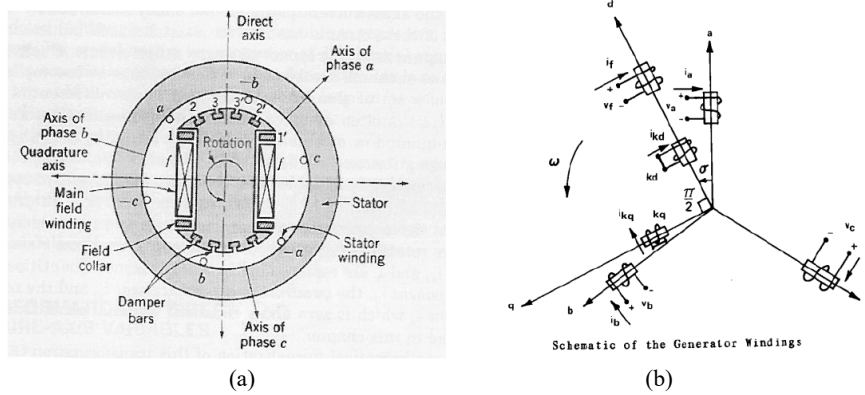


Fig-1: (a) A typical synchronous machine cross-section and (b) schematic of synchronous machine windings.

2. Write down the State Space (SS) model in expanded matrix form, use the symbols in the lecture notes (no values) for the following:
 - i. Case-1: Neglect the effects of the damping circuits in your SS model. Include only windings a, b, c, and f.

$$V = RI + \frac{d}{dt}(LI)$$

$$V = \begin{bmatrix} v_{aa} \\ v_{bb} \\ v_{cc} \\ v_f \end{bmatrix}, I = \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix}, I = \frac{d}{dt} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix}, R = \begin{bmatrix} r_s & 0 & 0 & 0 \\ 0 & r_s & 0 & 0 \\ 0 & 0 & r_s & 0 \\ 0 & 0 & 0 & r_f \end{bmatrix}, \text{ and } L = \begin{bmatrix} L_{aa} & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{bmatrix}$$

$$\begin{bmatrix} v_{aa} \\ v_{bb} \\ v_{cc} \\ v_f \end{bmatrix} = \begin{bmatrix} r_s & 0 & 0 & 0 \\ 0 & r_s & 0 & 0 \\ 0 & 0 & r_s & 0 \\ 0 & 0 & 0 & r_f \end{bmatrix} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix} + \frac{d}{dt} \left(\begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix} \begin{bmatrix} L_{aa} & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{bmatrix} \right)$$

- ii. Case-2: Account for the effects of the damping circuits in your SS model. Include all windings a, b, c, f, kd1, and kq1.

$$\begin{bmatrix} v_{aa} \\ v_{bb} \\ v_{cc} \\ v_f \\ v_{kd} \\ v_{kq} \end{bmatrix} = \begin{bmatrix} r_s & 0 & 0 & 0 & 0 & 0 \\ 0 & r_s & 0 & 0 & 0 & 0 \\ 0 & 0 & r_s & 0 & 0 & 0 \\ 0 & 0 & 0 & r_f & 0 & 0 \\ 0 & 0 & 0 & 0 & r_{kd} & 0 \\ 0 & 0 & 0 & 0 & 0 & r_{kq} \end{bmatrix} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \\ i_{kd} \\ i_{kq} \end{bmatrix} + \frac{d}{dt} \left(\begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \\ i_{kd} \\ i_{kq} \end{bmatrix} \begin{bmatrix} L_{aa} & L_{ab} & L_{ac} & L_{af} & L_{akd} & L_{akq} \\ L_{ba} & L_{bb} & L_{bc} & L_{bf} & L_{bkd} & L_{bkq} \\ L_{ca} & L_{cb} & L_{cc} & L_{cf} & L_{ckd} & L_{ckq} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} & L_{fk d} & L_{fk q} \\ L_{kda} & L_{kdb} & L_{kdc} & L_{kdf} & L_{kdkd} & L_{kd kq} \\ L_{kqa} & L_{kqb} & L_{kqc} & L_{kf f} & L_{kq kq} & L_{kq kq} \end{bmatrix} \right)$$

3. Write the state space model in the form using compact matrix notation, given in the course handouts. However, write the expanded form using expressions and numerical values for matrices A and B for:

$$V = RI + \frac{d}{dt}(LI), \quad V = RI + \omega \frac{dL}{d\theta} I + L \frac{dI}{dt}$$

$$\frac{dI}{dt} = \left(-L^{-1}R - L^{-1}\omega \frac{dL}{d\theta} \right) I + L^{-1}V$$

$$A = \left(-L^{-1}R - L^{-1}\omega \frac{dL}{d\theta} \right), \quad B = L^{-1}$$

- i. Case-1: Neglect the effects of the damping circuits in your SS model. Include only windings a, b, c, and f.

$$\begin{aligned} & \frac{d}{dt} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix} \\ &= \begin{pmatrix} L_{aa} + L_l & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} + L_l & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} + L_l & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{pmatrix}^{-1} \begin{bmatrix} r_s + r_l & 0 & 0 & 0 \\ 0 & r_s + r_l & 0 & 0 \\ 0 & 0 & r_s + r_l & 0 \\ 0 & 0 & 0 & r_f \end{bmatrix} \\ &- \begin{pmatrix} L_{aa} + L_l & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} + L_l & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} + L_l & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{pmatrix}^{-1} \omega \frac{d}{d\theta} \begin{pmatrix} L_{aa} + L_l & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} + L_l & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} + L_l & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{pmatrix} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \end{bmatrix} \\ &+ \begin{pmatrix} L_{aa} + L_l & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} + L_l & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} + L_l & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{pmatrix}^{-1} \begin{bmatrix} 0 \\ 0 \\ 0 \\ v_f \end{bmatrix} \end{aligned}$$

Expressions are given in the notes and coefficient values are given in the assignment.

- ii. Case-2: Account for the effects of the damping circuits in your SS model. Include all windings a, b, c, f, kd1, and kq1.

$$\begin{aligned}
 & \frac{d}{dt} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \\ i_{kd} \\ i_{kq} \end{bmatrix} \\
 &= \begin{bmatrix} L_{aa}+L_l & L_{ab} & L_{ac} & L_{af} & L_{akd} & L_{akq} \\ L_{ba} & L_{bb}+L_l & L_{bc} & L_{bf} & L_{bkd} & L_{bkq} \\ L_{ca} & L_{cb} & L_{cc}+L_l & L_{cf} & L_{ckd} & L_{ckq} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} & L_{fkd} & L_{fkq} \\ L_{kda} & L_{kdb} & L_{kdc} & L_{kdf} & L_{kdkd} & L_{kdqk} \\ L_{kqa} & L_{kqb} & L_{kqc} & L_{kqf} & L_{kqkd} & L_{kqqk} \end{bmatrix}^{-1} \begin{bmatrix} r_s + r_l & 0 & 0 & 0 & 0 & 0 \\ 0 & r_s + r_l & 0 & 0 & 0 & 0 \\ 0 & 0 & r_s + r_l & 0 & 0 & 0 \\ 0 & 0 & 0 & r_f & 0 & 0 \\ 0 & 0 & 0 & 0 & r_{kd} & 0 \\ 0 & 0 & 0 & 0 & 0 & r_{kq} \end{bmatrix} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \\ i_{kd} \\ i_{kq} \end{bmatrix} \\
 &- \omega \frac{d}{d\theta} \begin{bmatrix} L_{aa}+L_l & L_{ab} & L_{ac} & L_{af} & L_{akd} & L_{akq} \\ L_{ba} & L_{bb}+L_l & L_{bc} & L_{bf} & L_{bkd} & L_{bkq} \\ L_{ca} & L_{cb} & L_{cc}+L_l & L_{cf} & L_{ckd} & L_{ckq} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} & L_{fkd} & L_{fkq} \\ L_{kda} & L_{kdb} & L_{kdc} & L_{kdf} & L_{kdkd} & L_{kdqk} \\ L_{kqa} & L_{kqb} & L_{kqc} & L_{kqf} & L_{kqkd} & L_{kqqk} \end{bmatrix} \begin{bmatrix} i_{aa} \\ i_{bb} \\ i_{cc} \\ i_f \\ i_{kd} \\ i_{kq} \end{bmatrix} \\
 &+ \begin{bmatrix} L_{aa} & L_{ab} & L_{ac} & L_{af} \\ L_{ba} & L_{bb} & L_{bc} & L_{bf} \\ L_{ca} & L_{cb} & L_{cc} & L_{cf} \\ L_{fa} & L_{fb} & L_{fc} & L_{ff} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ v_f \end{bmatrix} \\
 &\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}
 \end{aligned}$$

PART II

Assuming that the machine is operating at its rated voltage, current, and power factor (overexcited) as a generator, calculate the necessary excitation field current assuming $v_f = r_f i_f = 338$ V. Also, assume the angle σ , between phase a-axis and the d-axis is equal to zero (meaning in Figs 1 & 2, the a-axis is aligned with the d-axis). In addition, consider the terminal voltage (to neutral) of phase a, V_a , to be the reference in the phasor diagram (meaning having a phase angle equal to zero).

At time $t=0.0$ the machine is connected to an infinite busbar where, a, b, and c phase voltages are given by:

$$v_a = \frac{20 \times 10^3}{\sqrt{3}} \sqrt{2} \cos(\omega t) \text{ Volts}$$

$$v_b = \frac{20 \times 10^3}{\sqrt{3}} \sqrt{2} \cos(\omega t - 2\pi/3) \text{ Volts}$$

$$v_c = \frac{20 \times 10^3}{\sqrt{3}} \sqrt{2} \cos(\omega t - 4\pi/3) \text{ Volts}$$

Assuming that the terminal voltage of the field winding is kept constant by the excitation control system at assuming $v_f = r_f i_f = 338$ V, and that the speed of the turbogenerator is maintained, by its prime mover, constant at its rated synchronous value:

1. Calculate the initial conditions (values at $t=0$ s) for i_a , i_b , i_c , i_f , i_{kd1} , i_{kq1}
 Since $t=0$, $\omega * t = 0$

$$I_a = \frac{S}{3 * |V_a|} [\cos^{-1}(pf)] = 19023.69 [25.84^\circ] A$$

$$i_{ao} = \sqrt{2} * |I_a| \cos(25.84^\circ)$$

$$i_{bo} = \sqrt{2} * |I_a| \cos(25.84^\circ - 120^\circ)$$

$$i_{co} = \sqrt{2} * |I_a| \cos(25.84^\circ - 240^\circ)$$

$$i_f = \frac{V_f}{r_f}, \quad i_{kd} = 0, \quad \text{and } i_{kq} = 0$$

2. Perform analysis for the following cases:
 - i. Neglect the effects of the damping circuits in your model. Calculate by means of numerical integration (MATLAB or Simulink) and *plot the profiles versus time over the first 30 cycles* for the following variables: i_a , i_b , i_c , i_f , and T_{em} .

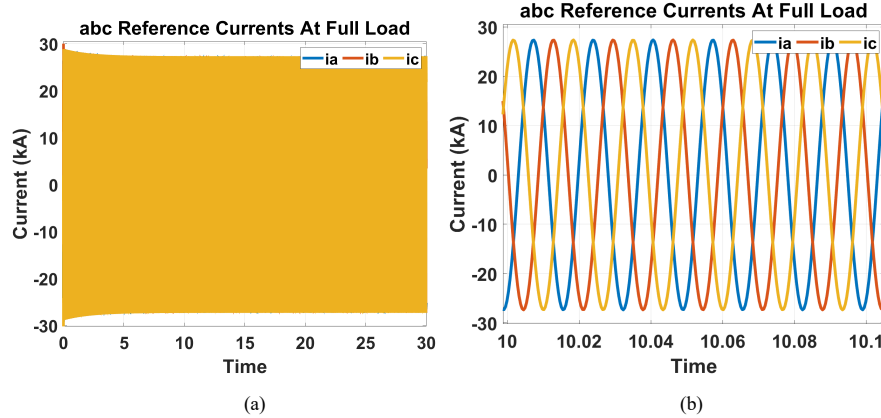


Fig-1: Phase currents

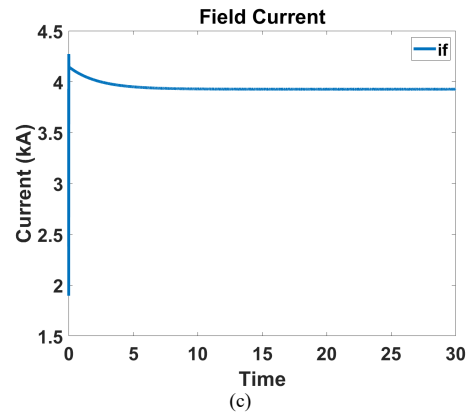


Fig-3: without damping case (a) Currents in abc frame of reference and (b) zoomed in (c) Field current

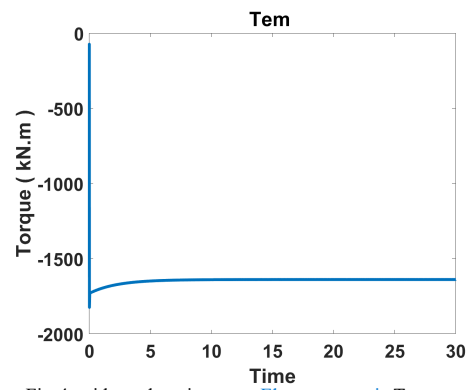


Fig-4: without damping case: [Electromagnetic](#) Torque.

- ii. Include the effects of the damping circuits in your model. Calculate by means of numerical integration (MATLAB or Simulink) and *plot the profiles versus time over the first 30 cycles* for the following variables: ia, ib, ic, if, ikd1, ikq1, and Tem

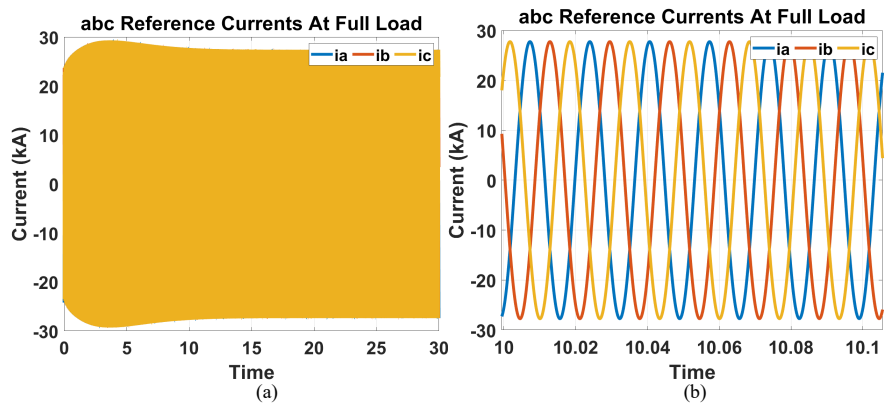


Fig-5 (a) Currents in abc frame of reference and (b) zoomed in

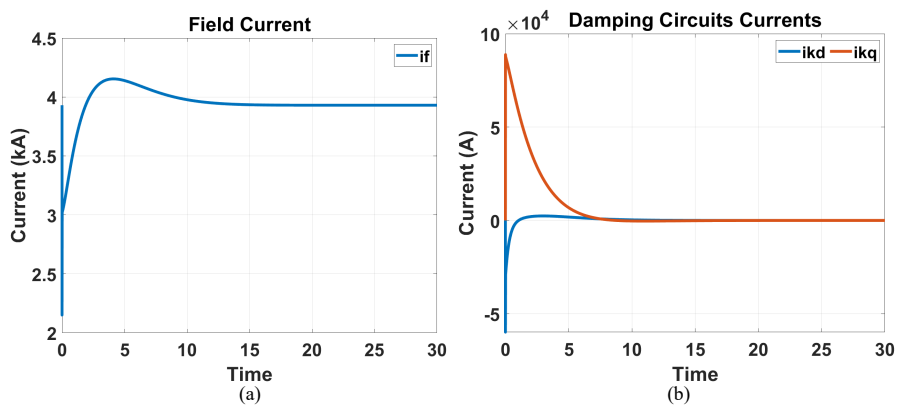


Fig-6: (a) Field current and (b) Damping currents.

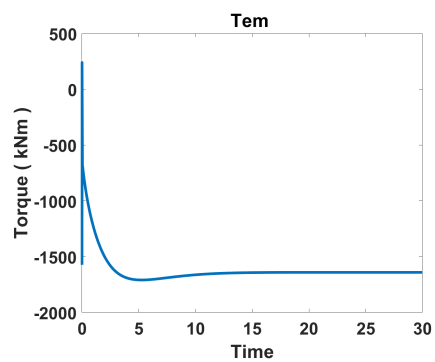


Fig-7: with damping case: T_{EM} Torque.

Appendix

MATLAB Pseudocode: Synchronous Machine State-Space Modeling

- **Define Initial Parameters**
 - Define constants: frequency f , angular velocity ω , voltage values (V_f , V_{Line} , V_{ph}), apparent power S , and power factor pf .
- **Compute Derived Quantities**
 - Calculate θ based on power factor.
 - Determine Z_l , r_l , X_l , and L_l .
 - Compute phase current I_a and phase angle.
 - Calculate initial currents: i_{fo} , i_{ao} , i_{bo} , i_{co} , i_{kdo} , i_{kqo} .
- **Set Simulation Parameters**
 - Define initial conditions iniCon for the ODE solver.
 - Specify the time span tspan .
- **Solve the State-Space Model**
 - Use `ode45` to solve the system of equations with the function `myode`.

```
iniCon = [iao;ibo;ico;ifo;ikdo;ikqo];  
tspan = [0 30];  
[t,x] = ode45(@myode, tspan, iniCon); % Solving for State Space  
Model (Synchronous Machine)
```

ODE Function (myode)

```
function dx = myode(t,x)
```

1. **Calculate angle θ based on time.**
2. **Define Parameters**
 - Define initialization of resistances, inductances, and other constants.
3. **Compute Inductance Matrix (\mathbf{L})**
 - Compute self and mutual inductances (L_{aa} , L_{bb} , L_{ab} , etc.) as functions of angle θ
 $= \omega t$.
 - Calculate derivatives of inductances (dL_{aa} , dL_{ab} , etc.).
4. **Define Resistance Matrix (\mathbf{R})**
 - Set up the resistance matrix with resistances r_s , r_l , r_f , r_{kd} , r_{kq} .
5. **Define System Matrices**
 - Compute inductance matrix \mathbf{L} .
 - Compute derivative of the inductance matrix $d\mathbf{L}$.
 - Calculate system matrices \mathbf{A} and \mathbf{B} .
6. **Define Input Vector (\mathbf{u})**
 - Set input voltages.

7. Compute State Derivative

- Calculate dx using the state-space equation: $dx=A \cdot x+B \cdot u$
- Return State Derivative (dx)

MATLAB Script solving the Synchronous Machine State-Space with Damping Effect

```
%% M3_SS_with_Damping_effect
clear all; close all; clc;

%% initial values calculations
f= 60;
w = 2*pi*f;
rf = 0.0860;
Vf = 338;
VLine = 20e3; %rms
Vph = 20e3/sqrt(3); %rms
S = 659e+06;
pf = 0.9;
theta = acos(pf); %in radian
IA = (S)/(3*Vph);
% Currents at t = 0
ifo = Vf/rf;
iao = sqrt(2)*IA*cos(-theta+pi);
ibo = sqrt(2)*IA*cos(-theta+pi-2*pi/3);
ico = sqrt(2)*IA*cos(-theta+pi-4*pi/3);
ikdo=0;
ikqo=0;
%% State Space Model (4th-Order Runge Kutta Method for ODEs)
iniCon = [iao;ibo;ico;ifo;ikdo;ikqo];
tspan = [0 30];
[t,x] = ode78(@myode, tspan, iniCon); % Solving for State Space Model (Synchronous Machine)

%% Plotting the results
Ia = x(:,1)*1e-3; %in kA
Ib = x(:,2)*1e-3; %in kA
Ic = x(:,3)*1e-3; %in kA
If = x(:,4);
Ik d = x(:,5);
Ik q = x(:,6);
figure(1)
plot(t , Ia , t , Ib , t , Ic);
legend('ia','ib','ic','NumColumns',3);xlabel('Time')
ylabel('Current (kA)')
title('abc Reference Currents At Full Load')
grid
figure(2)
plot(t ,If);
legend('if');xlabel('Time')
ylabel('Current (A)')
title('Field Current')
grid
figure(3)
plot(t , Ik d , t , Ik q);
legend('ikd','ikq');xlabel('Time')
ylabel('Current (A)')
title('Damping Circuits Currents')
grid
va = Vph*sqrt(2)*cos(w*t);
```

Formatted: Italian

```

vb = Vph*sqrt(2)*cos(w*t-2*pi/3);
vc = Vph*sqrt(2)*cos(w*t-4*pi/3);
p = va .* x (:,1) + vb .* x (:,2) + vc .* x (:,3) ;
tem = (p) ./ (w) ;
figure(4)
plot (t , tem/1e3 )
xlabel (" Time ")
ylabel (" Torque ( kNm ) ")
title (" Tem ")

```

```

function dx = myode(t,x)
    Vf = 338;
    Vline = 20e3; %rms
    S = 659e+06;
    pf = 0.9;
    that = (acos(pf));
    Zl = Vline^2/S;
    rl = Zl*cos(that);
    Xl = Zl*sin(that);
    Ll = Xl/(2*pi*60);
    n_m = (120*60)/4; %n_m = (120*f)/p
    w_m = n_m*(2*pi)*(1/60);
    theta_r = (w_m*t); % Rotor Angle

    rs = 7.4e-4; rf = 0.0860;
    rkd = 1.58e-4; rkq = 1.227e-4;
    Lsv = 0.05e-3; Lmv = 0.05e-3;
    Lsa = 1.95e-3; Lff = 444e-3;
    Lma = 0.80e-3; Lakdm = 0.447e-3;
    Lafm = 26.1e-3; Lakqm = 0.670e-3;
    Lfkdm = 5.05e-3; Lkdkd = 0.1254e-3;
    Lkdf = 6.29e-3; Lkqkq = 0.3762e-3;

    % type the inductance expression
    % function of the rotor angle (theta_r)
    Laa = Lsa+Lsv*cos(2*theta);
    Lbb = Lsa+Lsv*cos(2*theta-4*pi/3);
    Lcc = Lsa+Lsv*cos(2*theta-2*pi/3);
    Lab = -Lma+Lmv*cos(2*theta-2*pi/3);
    Lbc = -Lma+Lmv*cos(2*theta);
    Lac = -Lma+Lmv*cos(2*theta-4*pi/3);
    Laf = Lafm*cos(2*theta);
    Lbf = Lafm*cos(2*theta-2*pi/3);
    Lcf = Lafm*cos(2*theta-4*pi/3);
    Lakd = Lakdm*cos(2*theta);
    Lbkd = Lakdm*cos(2*theta-2*pi/3);
    Lckd = Lakdm*cos(2*theta-4*pi/3);
    Lakq = Lakqm*cos(2*theta+pi/2);
    Lbkq = Lakqm*cos(2*theta-2*pi/3+pi/2);
    Lckq = Lakqm*cos(2*theta-4*pi/3+pi/2);

    %the derivative of the inductances
    % function of the rotor angle (theta_r)
    dLaa = -2*Lsv*sin(2*theta);
    dLbb = -2*Lsv*sin(2*theta-4*pi/3);
    dLcc = -2*Lsv*sin(2*theta-2*pi/3);
    dLab = -2*Lmv*sin(2*theta-2*pi/3);
    dLbc = -2*Lmv*sin(2*theta);
    dLac = -2*Lmv*sin(2*theta-4*pi/3);
    dLaf = -2*Lafm*sin(2*theta);
    dLbf = -2*Lafm*sin(2*theta-2*pi/3);

```

```

dLcf = -2*Lafm*sin(2*theta-4*pi/3);
dLakd = -2*Lakdm*sin(2*theta);
dLbkd = -2*Lakdm*sin(2*theta-2*pi/3);
dLckd = -2*Lakdm*sin(2*theta-4*pi/3);
dLakq = -2*Lakqm*sin(2*theta+pi/2);
dLbkq = -2*Lakqm*sin(2*theta-2*pi/3+pi/2);
dLckq = -2*Lakqm*sin(2*theta-4*pi/3+pi/2);

R = [rs+rl      0      0      0      0      0;
      0      rs+rl      0      0      0      0;
      0      0      rs+rl      0      0      0;
      0      0      0      rf      0      0;
      0      0      0      0      rkd      0;
      0      0      0      0      0      rkq];

L = [Laa+Ll      Lab      Lac      Laf      Lakd      Lakq;
      Lab      Lbb+Ll      Lbc      Lbf      Lbkd      Lbkq;
      Lac      Lbc      Lcc+Ll      Lcf      Lckd      Lckq;
      Laf      Lbf      Lcf      Lff      Lfk      0;
      Lakd      Lbkd      Lckd      Lkdf      Lkdk      0;
      Lakq      Lbkq      Lckq      0      0      Lkqk];

dL = [ dLaa      dLab      dLac      dLaf      dLakd      dLakq;
       dLab      dLbb      dLbc      dLbf      dLbkd      dLbkq;
       dLac      dLbc      dLcc      dLcf      dLckd      dLckq;
       dLaf      dLbf      dLcf      0      0      0;
       dLakd      dLbkd      dLckd      0      0      0;
       dLakq      dLbkq      dLckq      0      0      0];

A = -inv(L)*(R+w*dL);
B = inv(L);
u = [0;0;0; Vf;0;0];
dx = A*x+ B*u;
end

```

State Space Equations

$$dI/dt = (V - R * I - w(dL/d\theta) * I)/L$$

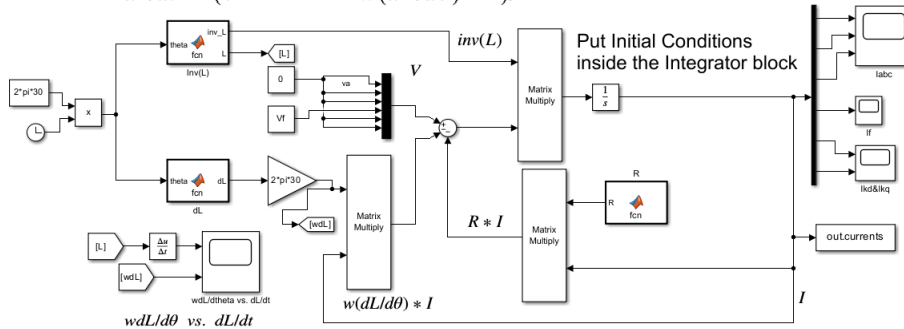


Fig-9: Simulink block diagram used to solve the system.

V. REFERENCES

- [1] A.A. Arkadan, and N.A. Demerdash, "Modeling of Transients in Permanent Magnet Generators with Multiple Damping Circuits Using the Natural abc Frame of Reference," IEEE Trans. on Energy Conversion, Vol. EC-3, No. 3, pp. 722-731, September 1988.
- [2] R. Krishnan. (2010). *Permanent Magnet Synchronous and Brushless DC Motor Drive*. Taylor and Francis Group.
- [3] Stephen J. Chapman. (2005). *Electric Machinery Fundamentals*. McGraw-Hill.
- [4] A.A. Arkadan EENG577 Class Notes, Colorado School of Mines.