

COLORADO SCHOOL OF MINES ELECTRICAL ENGINEERING DEPARTMENT

ENG 577

M1-A1 Assignment KEY

Multiple Choice: Each multiple-choice question is worth 10 point. Please choose the best answer for each question.

Q-1. A load has a voltage $V=208 \angle -30^{\circ} V$ and the current $I=2 \angle 20^{\circ} A$. The load power factor is about:


a) 0.24 Lagging b) 0.51 Leading c) 0.64 Leading d) None of the above

Solution:

 $Z=V/I = 208 \angle -30^{\circ}/2 \angle 20^{\circ} = 104 \angle -50^{\circ}$ $PF = \cos(-50^{\circ}) = 0.643 \text{ Leading}$

Q-2. The magnetic core shown has infinite permeability. The mutual inductance L_{12} is about:

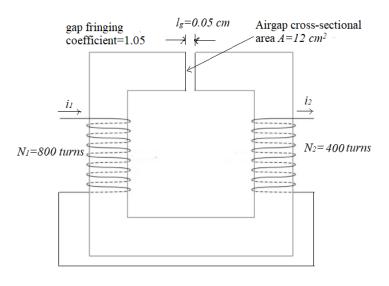a) L_{12} = 0.345 H **b)** L_{12} = 0.648 H **c)** L_{12} = 1.013 H **d)** None of the given answers



Solution:

$$R = \frac{l_g}{\mu_0 A_g} = \frac{0.0005m}{(4\pi x 10_-7)(1.05)(0.0012m^2)} = 316,000 \text{ A.T/Wb}$$


$$L_{12} = N_1 N_2 / R = 1.013 \text{ H}$$

Also, the self-inductances are:

$$L_{11} = N_1^2 / R = 2.025 \text{ H}$$

$$L_{22} = N_2^2 / R = 0.506 \text{ H}$$

Q-3. Consider the system shown.

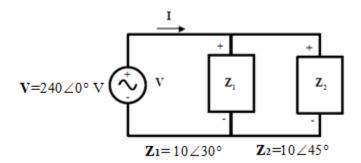

The system power factor is about:

a) PF=0.89 Lead. b) PF=0.37 Lag. c) PF= 0.79 Lag. d) None of the given answers

Solution:

The current I_1 in load Z_1

$$I_1 = \frac{240 \angle 0^{\circ} \text{ V}}{10 \angle 30^{\circ} \text{ A}} = 24 \angle -30^{\circ} \text{ A}$$

The current I2 in Load 2 is

$$I_2 = \frac{240 \angle 0^{\circ} \text{ V}}{10 \angle 45^{\circ} \text{ A}} = 24 \angle -45^{\circ} \text{ A}$$


Therefore the total current from the source is

$$I = I_1 + I_2 = 24 \angle -30^{\circ} A + 24 \angle -45^{\circ} A = 47.59 \angle -37.5^{\circ} A$$

The power factor supplied by the source is

$$PF = \cos \theta = \cos(37.5^{\circ}) = 0.793 \text{ lagging}$$

Q-4. Consider the system shown.

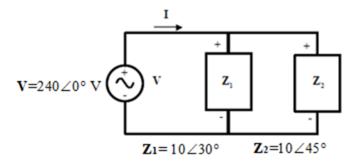

The total apparent power S supplied by the source is about:


a) 5,760 VA **b)** 11,420 VA **c)** 4,073 VA **d)** None of the above

Solution

S=VI= (240V)(47.59A)=11,420 VA

Q-5. The system shown has a reluctance R = 252 kA.t/Wb. The current that will produce a flux of 0.001 Wb is about:

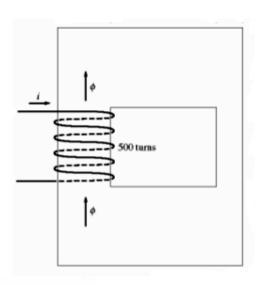
a) 2A b) 0.5 A c) 1.5A d) None of the given answers



Solution:

 $F = \phi R = (0.001 \text{ Wb})(252 \text{ kA} \cdot \text{t/Wb}) = 252 \text{ A T}$ and the required current is I=F/N=252/500=0.5 A

Q-6. The load power factor is about:

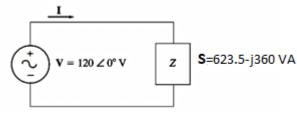


a) PF=0.87 Lead. b) PF=0.43 Lead. c) PF=0.5 Lag. d) None of the above

Solution

 $\overline{\theta = \tan^{-1}(Q/P)} = \tan^{-1}(360/623.5) = 30^{\circ}$

PF= $\cos(\theta)$ =0.866 Leading since it supplies reactive power.

Q-7. The load current **I** is about:

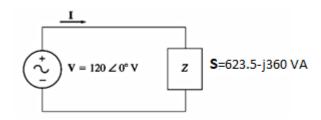

- **a)** $I = 6 \angle 30^{\circ} \text{ A}$ **b)** $I = 16 \angle 43^{\circ} \text{ A}$ **c)** $I = 9 \angle 15^{\circ} \text{ A}$
- **d)** None of the above

Solution

S=VI*=623.5-j360=720∠30°

 $I=(S/V)^* = 6 \angle 30^\circ A$

Q-8. The wire moving as shown has an induced voltage e_{ind} of about:


- a) e_{ind} = 0.613 V positive up
- **b)** e_{ind} = 0.613 V positive down **c)** e_{ind} = 0.35 V positive up

d) e_{ind} = 0.35 V positive down

$$e_{ind} = (vxB).I = vBl \cos 40^{\circ} = (10m/s)(0.4T)(0.2m) \cos 40^{\circ} = 0.613 \text{ V}$$
 positive up

Q-9. Consider the wire shown below which carries current in the presence of a magnetic field. The magnetic flux density is 0.25 T, directed into the page. If the wire is 10 m long and carries 0.5 A of current in the direction from the top of the page to the bottom of the page, the magnitude and direction of the force induced on the wire is about:

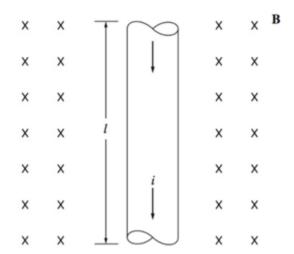- a) 0.125 N directed to the right
- **b)** 1.25 N directed to the right **c)** 12.5 N directed to the left
- **d)** None of the given answers



Solution


The direction of the force is given by the right-hand rule as being to the right. The magnitude is given by

$$F = ilB \sin \theta$$


= (0.5 A)(1 0 m)(0.25 T) sin 90° = 1.25 N directed to the right.

Q-10. The magnetic cores shown have infinite relative permeability and no fringing effects in the air gaps. Also, assume N1>N2. If the magnetic core for both designs are identical, except the way the coils are connected. If Core-1 mutual inductance is LM1, and Core-2 mutual inductance is LM2, the following can be stated:

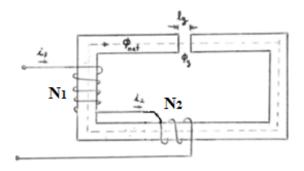- **a**) $L_{M1} > L_{M2}$
- **b**) $L_{M1} < L_{M2}$
- **c)** $L_{M1} = L_{M2}$
- **d)** None of the given answers



Core-1 Design

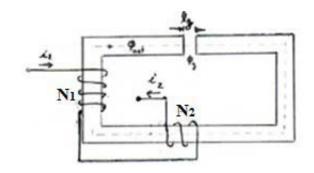

Core-2 Design

Solution

 $L_{M1}=L_{M2}=N1 \ N2/R$