



COLORADO SCHOOL OF MINES
ELECTRICAL ENGINEERING
DEPARTMENT
ENG 577
M2 Project KEY

1. For the system shown, find the equivalent electric circuit and draw it.

Solution:

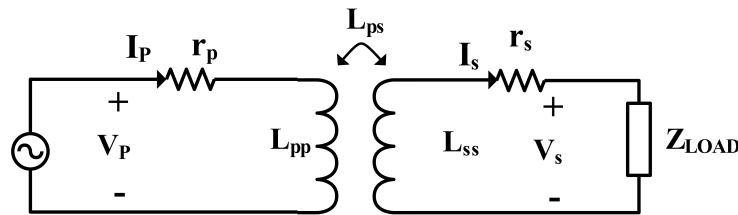


Figure 1 – Equivalent Circuit.

2. Write the governing voltage equations for $v_1(t)$ and $v_2(t)$ in terms of currents $i_1(t)$ and $i_2(t)$ given $Z_{Load}=R_L + jX_L$ and coils 1 and 2 resistances R_1 and R_2 (use symbols only).

Solution:

The transformer state-space model is expressed as [1],

$$\bar{V} = \bar{R} \cdot \bar{I} + \frac{d\bar{\lambda}}{dt}$$

Where λ_j is the flux linkage (obtained as $\lambda_j = \sum_{k=1}^n L_{jk} \cdot i_k$). for winding jth, and n is the number of coils. Therefore, the equation can be rewritten as,

$$\bar{V} = R \cdot \bar{I} + L \cdot \frac{d\bar{I}}{dt}$$

Using the equivalent electric circuit, the following equation can be obtained:

$$v_1 = r_1 \cdot i_1 + \frac{d}{dt} (L_{11} \cdot i_1 + M \cdot i_2)$$

$$v_2 = r_2 \cdot i_2 + \frac{d}{dt} (L_{22} \cdot i_2 + M \cdot i_1)$$

Using the voltage equations, the state space model can be expressed as matrices:

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} r_1 & 0 \\ 0 & r_2 \end{bmatrix} \cdot \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} L_{pp} & M \\ M & L_{ss} \end{bmatrix} \cdot \frac{d}{dt} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

The secondary voltage is related to the load, Z_{load} , as $v_s = Z_{load} \cdot i_s$ where Z_{load} is represented by r_l and L_l . As such, the equation above can be rearranged and can be used to solve for the current vector \vec{I} as follows:

$$\frac{d}{dt} \begin{bmatrix} i_p \\ i_s \end{bmatrix} = - \begin{bmatrix} L_{pp} & M \\ M & (L_{ss} + L_l) \end{bmatrix}^{-1} \cdot \begin{bmatrix} r_p & 0 \\ 0 & (r_s + r_l) \end{bmatrix} \cdot \begin{bmatrix} i_p \\ i_s \end{bmatrix} + \begin{bmatrix} L_{pp} & M \\ M & (L_{ss} + L_l) \end{bmatrix}^{-1} \cdot \begin{bmatrix} v_p \\ 0 \end{bmatrix}$$

3. Use MATLAB to plot the current $i_1(t)$ and $i_2(t)$, assuming the following: $f=60$ Hz, $v_1(t)=120 \cos(\omega t)$ & $Z_{Load}=20 \angle +30^\circ \Omega$, $R_1=0.2 \Omega$ and $R_2=0.4 \Omega$.

Solution:

First, the inductances (self and mutual) are calculated using the transformer parameters available.

```
N1 = 800;
N2=400;
Gaplength = .0005;
area = 0.0012;
gapCoef = 1.05;
mu0 = 4*pi*1e-7;
Relc = (len)/(area*gapCoef*mu0);
L11 =N1^2/Relc;
L22 = N2^2/Relc;
L12 = (N2*N1)/Relc;
```

Second, find the load parameters. Where the load is $Z_{Load} = 20 \angle 30$

```
RL = 20*cosd(30);
Ll = (20*sind(30))/((2*pi*60)); % Ll = XL/(2*pi*f)
```

Finally, put everything together and build the SS script to solve for the currents based in the equations above. First, using MATLAB ODE45 function.

```
%% State Space Model (4th-Order Runge Kutta Method for ODEs)
tspan = [0 1]; % integrates the system of differential equations from 0 to 0.0667
                % time of running. Note: the time is longer to get accurate results for the current values.
iniCon = [0;0]; %initial conditions or initial current value
[t,x] = ode45(@myode, tspan, iniCon); %
Is = rms(x(:,2));
Ip = rms(x(:,1));
plot(t,x(:,1),t,x(:,2));
legend('i1','i2')
xlabel('Time')
ylabel('Current [Amps]')
title('Kutta Method for ODEs')
grid
function dx = myode(t,x)
    %inductances calculations
    N1 = 800;
    N2=400;
    len = .0005;
    area = 0.0012;
    gapCoef = 1.05;
    mu0 = 4*pi*1e-7;
    Relc = (len)/(area*gapCoef*mu0);
    L11 = N1^2/Relc;
    L22 = N2^2/Relc;
    L12 = (N2*N1)/Relc;
    %Load parameters calculations
    RL = 20*cosd(-30);
    LI = (20*sind(30))/((2*pi*60));
    %windings' resistance values
    R1 =0.2;
    R2 = 0.4;
    R = [R1 0;0 R2+RL];
    L = [L11 L12;L12 L22+LI];
    Vp = 120;
    A = -inv(L)*R;
    B = inv(L);
    K = [Vp;0];
    u = K*sin(377.*t+(pi/2));

    dx = A*x+ B*u;
end
```

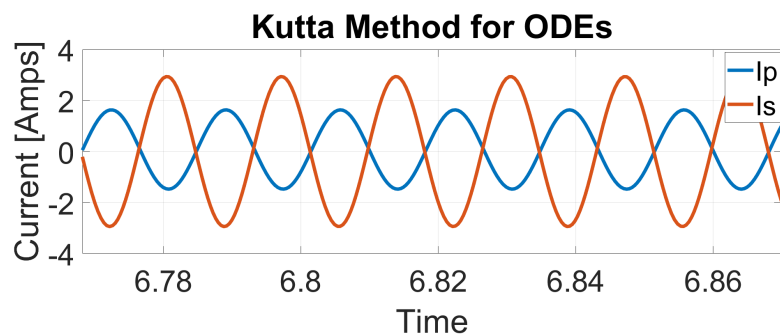


Figure 2 – Transformer Primary and Secondary Current

Or using Euler's Method:

```
n=60;
h=0.000167;           % step size
t=0:h:1;               % time of running. Note: the time is longer to get
                        % accurate results for the current values.
x=zeros(2,length(t)); % initialize the state vector size
K=[1;0];
A=-inv(L)*R;
B=inv(L);
u=K*Vp;
SS=A*x+ B*u*sin(377*t+pi/2);
dx=@(t,x)(A*x+ B*u*sin(377.*t));
%% State Space Model (Euler's Method)
%
for i=1:(length(t)-1)
    t(i+1)=t(i)+h;
    x(:,i+1)=x(:,i)+ h*dx(t(i),x(:,i));
end
plot(t,x(1,:),t,x(2,:))
legend({'I1','I2'})
xlabel('time')
ylabel('Current Values')
title('Euler Method')
Is=rms(x(2,:));
Ip=rms(x(1,:));
```

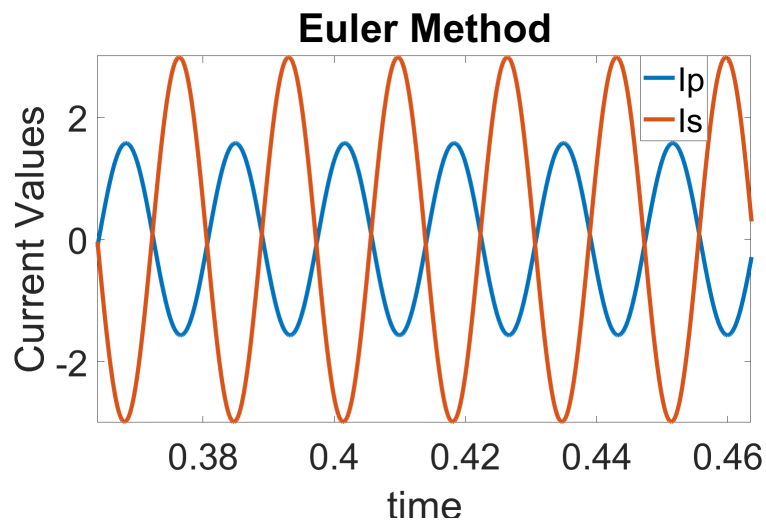


Figure 3 – Transformer Primary and Secondary Current

Or using MATLAB/Simulink

State Space Equations

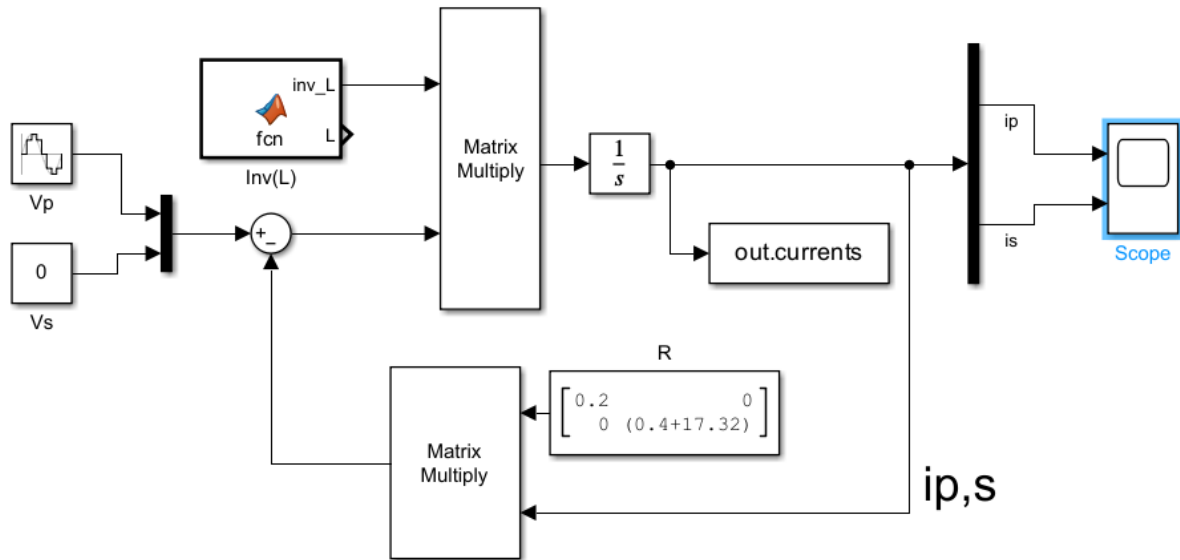
$$dI/dt = (V - R \cdot I) / L$$


Figure 4 – Transformer Primary and Secondary Current

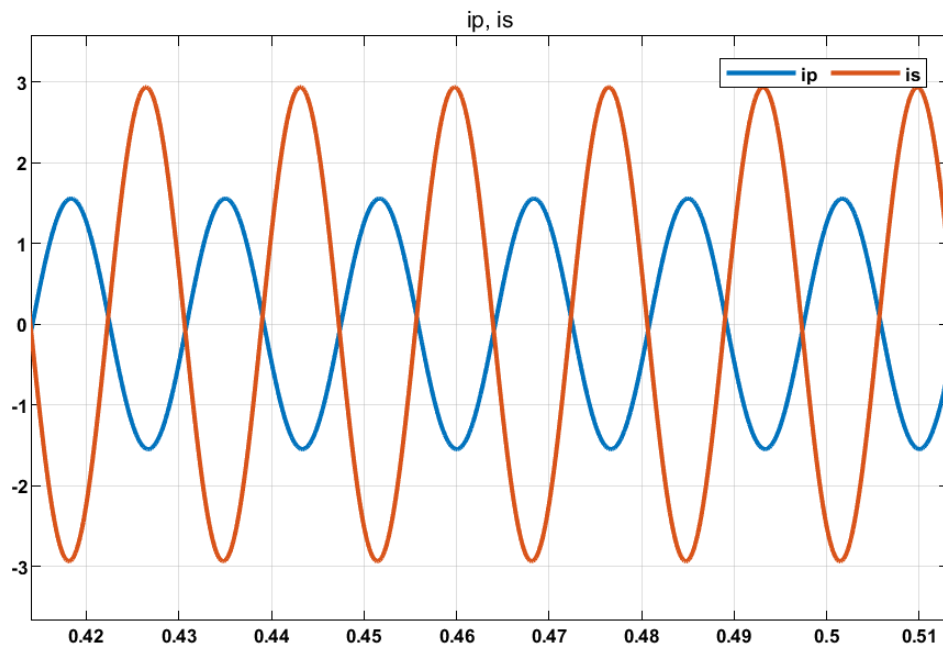


Figure 5 – MATLAB/Simulink Transformer Primary and Secondary Current

4. Calculate the load real, reactive, and complex powers and write down the values.

The load real power can be found by multiplying the current squared by the resistance of the load.

$$P = I_{2,rms}^2 \cdot r_l = 77.1 \text{ W}$$

With real power calculated, apparent power can be determined by using the power triangle.

$$S = \frac{P}{\cos(30)} = \frac{P}{PF} = 88.9 \text{ VA}$$

Finally, the reactive power can be found using current and impedance.

$$Q = \sqrt{S_L^2 - P_L^2} = I_{2,rms}^2 \cdot X_{Ll} = S \cdot \sin(30) = 44.5 \text{ VAR}$$

[1] Colorado School of Mines, EENG577 Class Notes, January, 2023.

[2] R. A. Almazmomi, M. A. Gutierrez-McCoy and A. A. Arkadan, "Transformer EM-FL-PSO Design Optimization," *2021 IEEE Green Technologies Conference (GreenTech)*, Denver, CO, USA, 2021, pp. 430-434, doi: 10.1109/GreenTech48523.2021.00073.