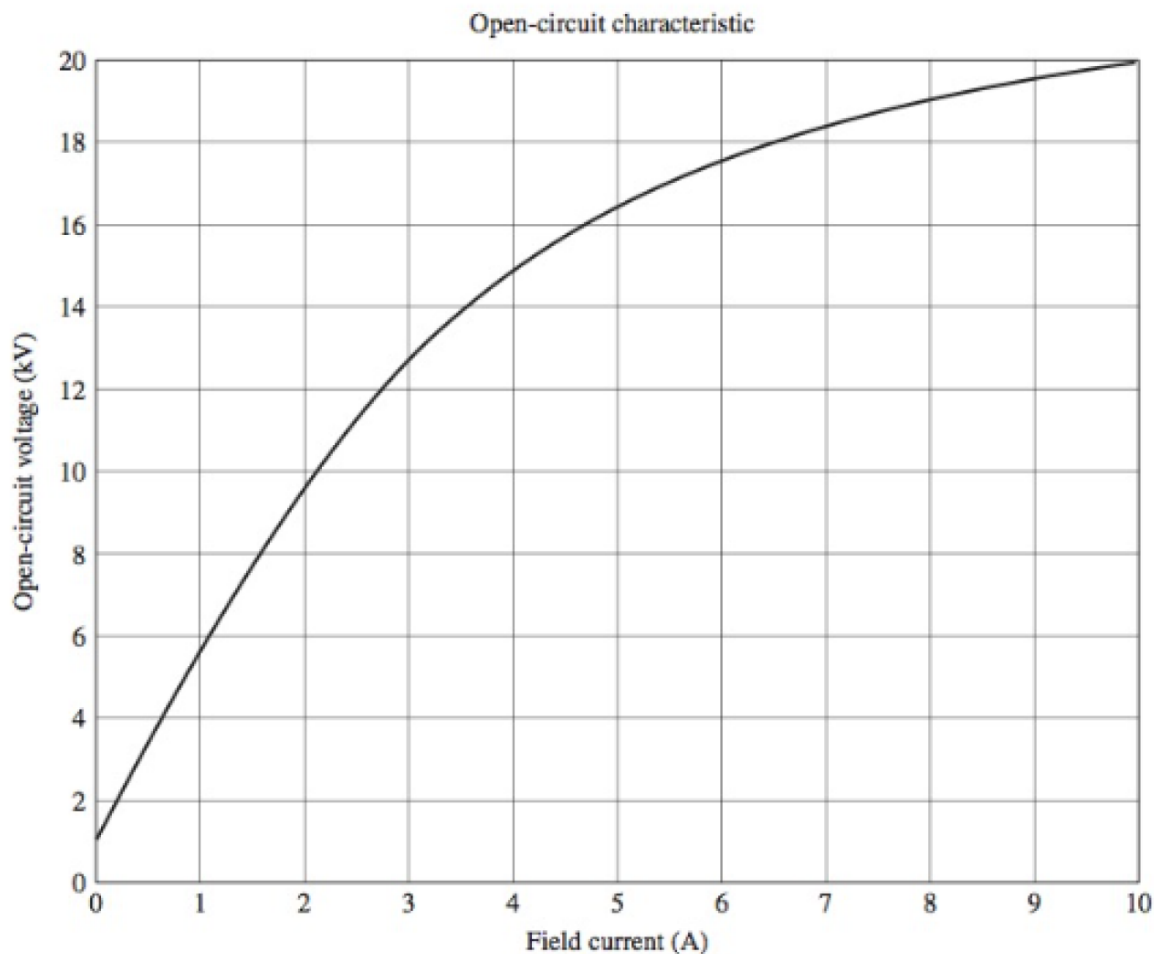


**COLORADO SCHOOL OF MINES****ELECTRICAL ENGINEERING DEPARTMENT****EENG577 Advanced Electric Machine Dynamics for Smart-Grid Systems****M3 Assignment 1: Synchronous Generators****4-2 (a-d, 20 pts)**

A 13.8-kV, 50-MVA, 0.9-power-factor-lagging, 60-Hz, four-pole Y-connected synchronous generator has a synchronous reactance of 2.5Ω and an armature resistance of 0.2Ω . At 60 Hz, its friction and windage losses are 1 MW, and its core losses are 1.5 MW. The field circuit has a dc voltage of 120 V, and the maximum I_F is 10 A. The current of the field circuit is adjustable over the range from 0 to 10 A. The OCC of this generator is shown in Figure P4-1.

**Figure P4-1**

Open-circuit characteristic curve for the generator in Problem 4-2.

- How much field current is required to make the terminal voltage V_T (or line voltage V_L) equal to 13.8 kV when the generator is running at no load?
- What is the internal generated voltage E_A of this machine at rated conditions?
- What is the phase voltage V_ϕ of this generator at rated conditions?
- How much field current is required to make the terminal voltage V_T equal to 13.8 kV when the generator is running at rated conditions?

4-6 (a-d, 20 pts)

The internal generated voltage E_A of a 2-pole Δ -connected, 60 Hz, three phase synchronous generator is 14.4 kV, and the terminal voltage V_T is 12.8 kV. The synchronous reactance of this machine is 4Ω , and the armature resistance can be ignored.

- If the torque angle of the generator $\delta = 18^\circ$, how much power is being supplied by this generator at the current time?
- What is the power factor of the generator at this time?
- Sketch the phasor diagram under these circumstances?
- Ignoring losses in this generator, what torque must be applied to its shaft by the prime mover at these conditions?

4-7 (a-c, 15 pts)

A 100-MVA, 14.4-kV, 0.8-PF-lagging, 50-Hz, two-pole, Y-connected synchronous generator has a per-unit synchronous reactance of 1.1 and a per-unit armature resistance of 0.011.

- What are its synchronous reactance and armature resistance in ohms?
- What is the magnitude of the internal generated voltage E_A at the rated conditions? What is its torque angle δ at these conditions?
- Ignoring losses in the generator, what torque must be applied to its shaft by the prime mover at full load?

4-8 (a-e, 25 pts)

A 200-MVA, 12-kV, 0.85-PF-lagging, 50-Hz, 20-pole, Y-connected water turbine generator has a per-unit synchronous reactance of 0.9 and a per-unit armature resistance of 0.1. This generator is operating in parallel with a large power system (infinite bus).

- What is the speed of rotation of this generator's shaft?
- What is the magnitude of the internal generated voltage E_A at rated conditions?
- What is the torque angle of the generator at rated conditions?
- What are the values of the generator's synchronous reactance and armature resistance in ohms?
- If the field current is held constant, what is the maximum power possible out of this generator? How much reserve power or torque does this generator have at full load?